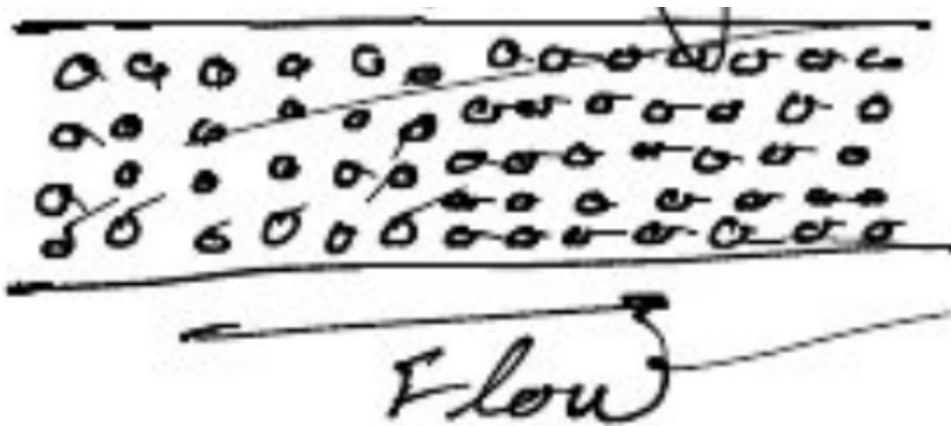


## Lecture 2 - Basic Electronics and Components


### I. Basic electronics theory: Current, Resistance and Voltage

- Electron:
  - $e^-$
  - "A tiny bit of charge"
- Current:
  - How much charge passes a point per second.




... think of it as a tube full of tiny balls.

- Resistance:

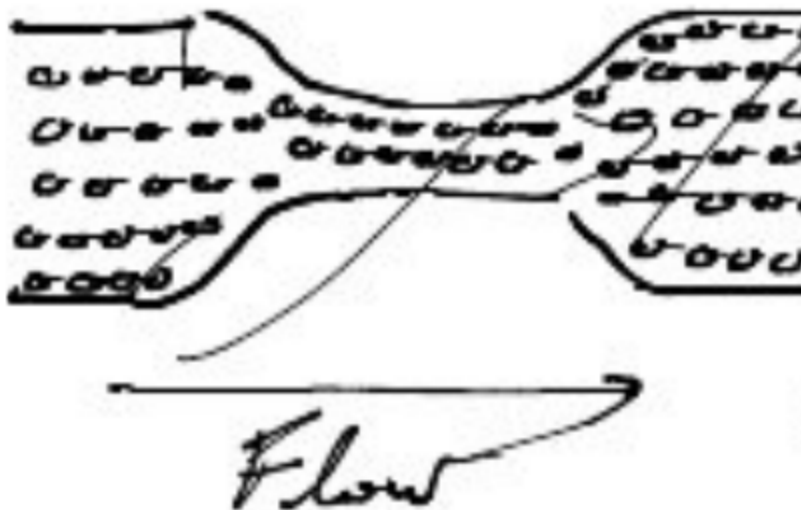


A limitation to the amount of charge that can pass through a point.

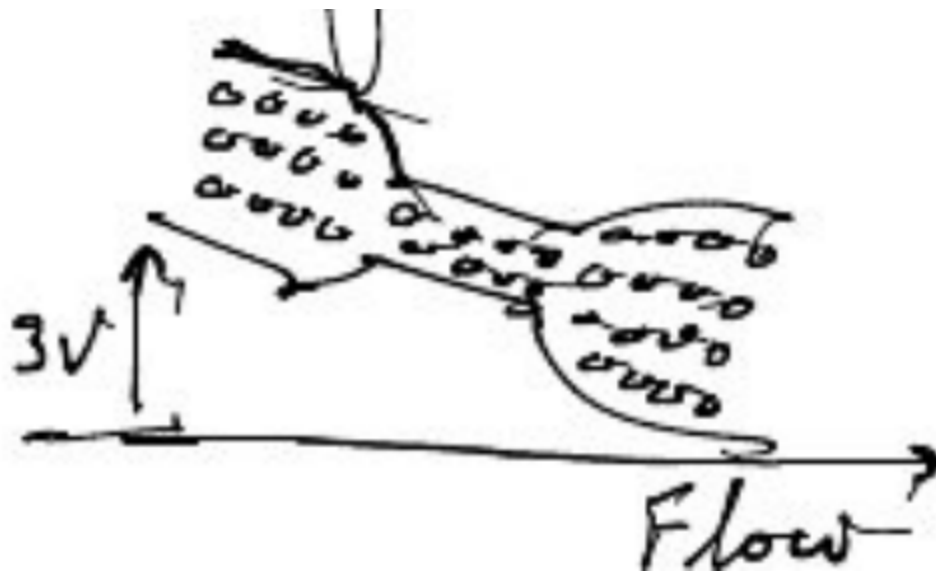- Voltage:
  - Electrical potential difference between two points in a circuit...



However... voltage is relative!

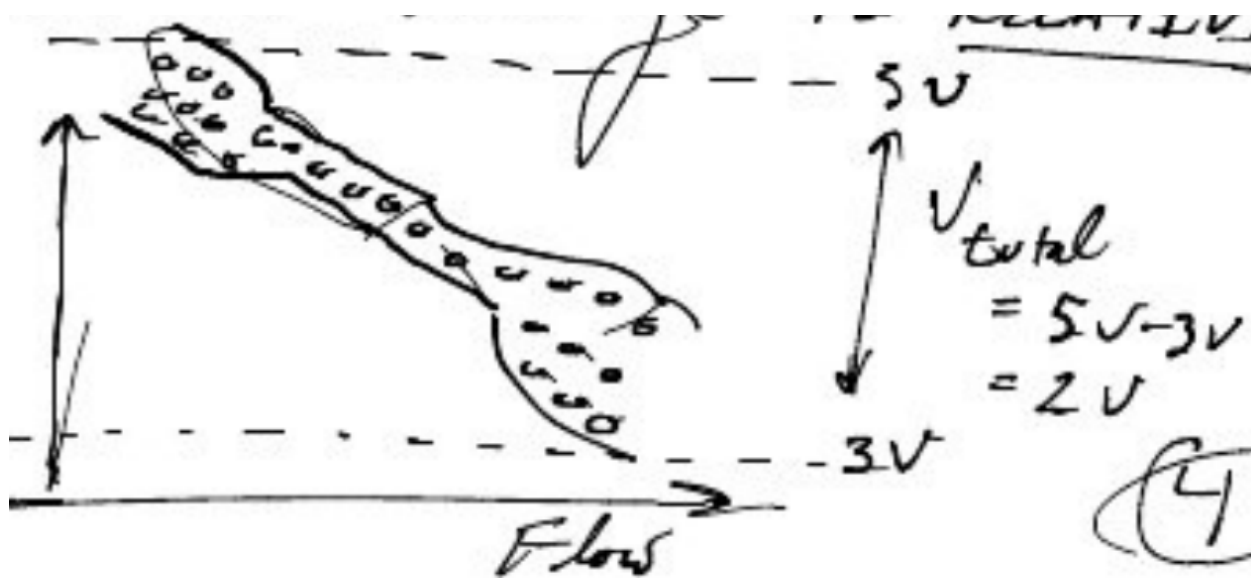

## II. Ohm's Law

- Relationship between current, voltage and resistance.
- $V = IR$ 
  - Where "V" is voltage
  - "I" is current
  - "R" is resistance

## III. Electronic Component Identification Guide

- Resistors:


- Symbol:



- Reduces current flow
- Keeps stuff from blowing up (among other things)
- Most common component.

- Capacitors:

- Symbol:

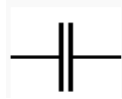

- Stores up charge and releases it quickly over time
- Does not produce charge!
- Good for "smoothing" signals
- Stabilizes voltage and power flow.

- Diode:

- Symbol:



- Only allows electrons to flow one way
- Prevents "slosh-back" that can damage components "up stream".

- LEDs:


- Symbol:



- A type of diode that produces light when electricity passes through.

- Transistor:

- Symbol:

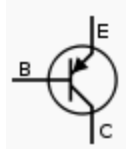

- Very important!
    - Switches that use small currents to control big currents
    - Video: <https://www.youtube.com/watch?v=IcrBqCFLHIY>
    - Acts as an on / off switch
      - Binary!
      - Can perform logical operations!
  - I.C.
    - Integrated circuit
    - An electronic circuit formed on semiconducting material

Chips, processors, timers, gates ... arduino!